

Bipolar Junction Calculation HW (18 Points)


(jas, BJT Calculation HW.docx, 2/26/2024)

1. Determine the base current I_B of Q1 in the adjacent circuit, given $V_{BE} = 0.7$ V. (Hint: Your answer should be between 20 and 30 μ A.) (1 point.)

$$I_B = \frac{3 - 0.7 \text{ V}}{100 * 10^3 \Omega} = 23 \mu\text{A}$$

$$I_B = 23 \mu\text{A}$$

v

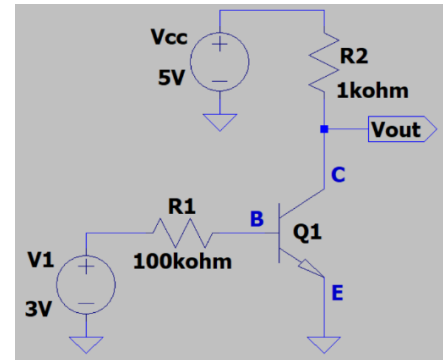


2. Determine the collector current I_C of Q1 in the adjacent circuit given $V_{BE} = 0.7$ V and $\beta = 100$. (Hint: Your answer should be between 1.8 and 2.2 mA.) (2 points.)

$$I_B = \frac{2.7 - 0.7 \text{ V}}{100 * 10^3 \Omega} = 20 \mu\text{A}$$

$$I_C = \beta I_B = 100(20 \mu\text{A}) = 2000 \mu\text{A} = 2.0 \text{ mA}$$

$$I_C = 2.0 \text{ mA}$$

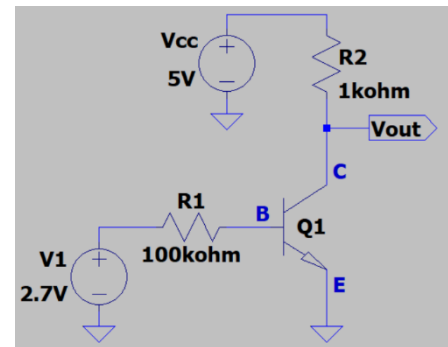

3. Determine the following for the adjacent circuit given $\beta = 53$ for Q1. (Hint: I_B should be between 40 and 50 μ A.) (3 points total.)


- a. V_{out} . (2 points.)

$$I_B = \frac{3 - 0.7 \text{ V}}{51 * 10^3 \Omega} = 45 \mu\text{A}$$

$$I_C = 53(45 \mu\text{A}) = 2.39 \text{ mA}$$

$$V_{CE} = V_o = V_{CC} - V_{R2} = 5\text{V} - 2.39 \text{ mA}(2\text{k}\Omega) = 4.78 \text{ V}$$

$$V_{out} = 4.78 \text{ V}$$

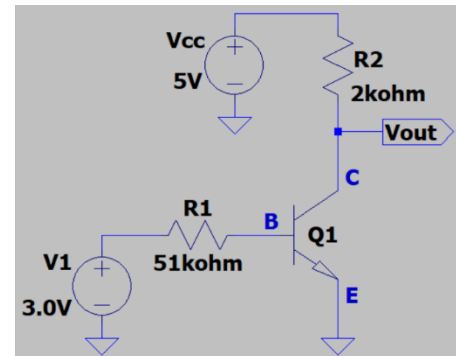

- b. The region of operation for Q1, with the choices being Cutoff, Circuit Saturation, or the Active Region. (1 point.)

$$V_{CE} > 0.3\text{V} \rightarrow \text{active region}$$

4. Determine the following for the adjacent circuit given $\beta = 100$ for Q1. (Hint: I_B should be between 25 and 35 μA .) (3 points total.)

a. V_{out} . (2 points.)


$$I_B = \frac{3.7 - 0.7 \text{ V}}{100 * 10^3 \Omega} = 30 \mu\text{A}$$

$$I_C = 100(30 \mu\text{A}) = 3.0 \text{ mA}$$

$$V_{R2} = 3\text{mA} * 1\text{k}\Omega$$

$$V_{BE} = V_{\text{out}} = V_{CC} - V_{R2} = 2 \text{ V}$$

$$V_{\text{out}} = 2 \text{ V}$$

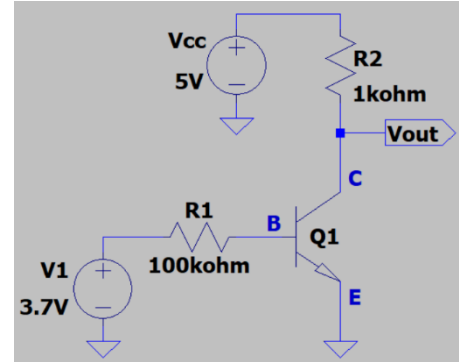


- b. The region of operation for Q1, with the choices being Cutoff, Circuit Saturation, or the Active Region. (1 point.)

$$V_{BE} = 2 \text{ V} < 0.7 \text{ V} \rightarrow \text{Active}$$

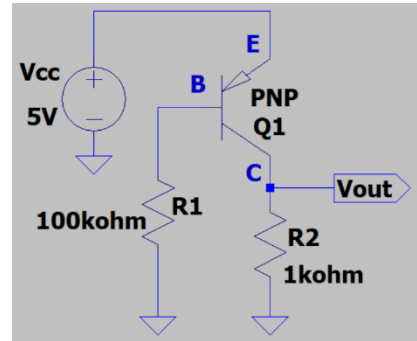5. Determine the base current I_B of Q1 in the adjacent circuit given $V_{EB} = 0.7 \text{ V}$ and noting that conventional current is considered negative when flowing out of a transistor terminal. (Hint: Your answer should have a magnitude between 40 and 50 μA .) (1 point.)

$$I_B = \frac{V_{CC} - V_{EB}}{R1} = \frac{5 - 0.7}{100 \text{ k}\Omega} = 43 \mu\text{A}$$

$$I_B = -43 \mu\text{A} \text{ (flowing out of base)}$$




6. Determine the collector current I_C of Q1 in the adjacent circuit given $V_{BE} = 0.7 \text{ V}$, $\beta = 110$, and noting that conventional current is considered negative when flowing out of a transistor terminal. (Hint: Your answer should have a magnitude between 4.2 and 4.6 mA .) (2 points.)

$$I_B = \frac{V_{CC} - V_{BE}}{R1} = \frac{4.7 - 0.7 \text{ V}}{100 * 10^3 \Omega} = 40 \mu\text{A}$$

$$I_C = \beta I_B = 110(40 \mu\text{A}) = 4.4 \text{ mA}$$

$$I_C = 4.4 \text{ mA}$$

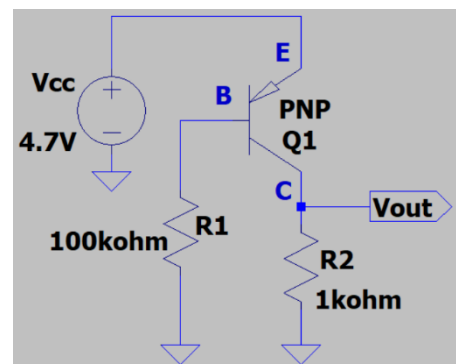

7. Determine the following for the adjacent circuit given $\beta = 95$ for Q1. (Hint: $|I_B|$ should be between 18 and 25 μA .) (3 points total.)

a. V_{out} . (2 points.)


$$V_{BE} = 0.7 V$$

$$I_B = \frac{5 - 0.7 V}{200 * 10^3 \Omega} = 21.5 \mu A$$

$$I_C = \beta I_B = 95(21.5 \mu A) = 2.04 mA$$

$$V_o = I_C(R_2) = 2.04 mA(1 k\Omega) = 2.04 V$$

$$V_o = 2.04 V$$

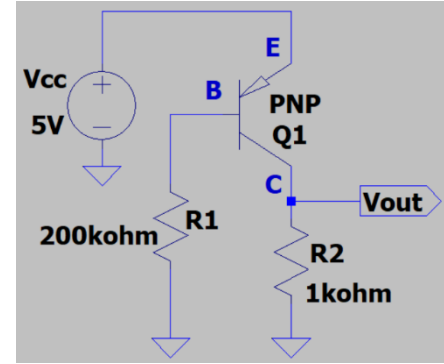

- b. The region of operation for Q1, with the choices being Cutoff, Circuit Saturation, or the Active Region. (1 point.)

$$V_{CE} = V_{CC} - V_o = 5V - 2.04V = 2.96V \rightarrow \text{active region}$$

8. Determine the following for the adjacent circuit given $\beta = 60$ for Q1. (Hint: $|I_B|$ should be between 30 and 50 μA .) (3 points total.)

a. V_{out} . (2 points.)


$$V_{BE} = 0.7 V$$

$$I_B = \frac{4.7 - 0.7 V}{100 k\Omega} = 40 \mu A$$

$$I_C = \beta I_B = 60(40 \mu A) = 2.4 mA$$

$$V_o = I_C(R_2) = 2.4 mA(1.91 k\Omega) = 4.58 V$$

$$V_o = 4.58 V$$

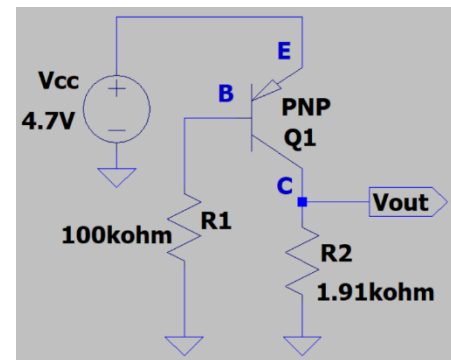

- b. The region of operation for Q1, with the choices being Cutoff, Circuit Saturation, or the Active Region. (1 point.)

$$V_{CE} = 5V - 4.58 V = 0.416 V > 0.3 \rightarrow \text{active}$$